

**Shyampur Siddheswari Mahavidyalaya**

**B.SC. Sem1(Internal Test)- 2019**

**COMPUTER SCIENCE (Hons.)**

**CC1**

**Total Marks-30**

**Time- 1Hr.**

1. Answer Any four questions. 1.5 x 4=6
  - (a) Find out the decimal equivalent for the binary number 11011.101?
  - (b) State the De Morgan's theorem?
  - (c) What is a digital signal? Give two examples of digital signal?
  - (d) Convert the decimal number 52 to binary?
  - (e) Convert the Gray code 1101 to binary.
  - (f) What is AOI logic?
  - (g) What is combinational circuit? Give examples.
  
2. Answer any four questions. (6 x 4=24)
  - (a) Draw the logic diagram and write the truth table of a full-adder.  
  
Draw the logic diagram of a half subtractor. 2+2+2=6
  - (b) What is universal Gates? Describe how AOI logic is described by these  
  
Gates? 2+4=6
  - (c) How is sequential circuit different from combinational circuit?  
  
What is multiplexer? Draw the circuit and working of a 4:1 MUX . 1+2+3
  - (d) Convert the binary number 110101.101010 to octal equivalent?  
  
Convert the binary number 010111100011 to its equivalent hexadecimal number.  
  
Convert decimal number 105.15 to binary . 2+2+2
  - (e) Realize the X-OR function using AOI logic, NAND logic and NOR logic. 2+2+2
  - (f) What is XS-3 code? Convert the binary 1001 to the Gray code. Explain error detecting code?  
  
2+2+2
  - (h) Draw the logic diagram of a full subtractor. Write the truth table and explain it. 3+3